



SUBJECT


Noise.

NAME

DATE


REVISION DATE

Consider a Resistor at a temperature T

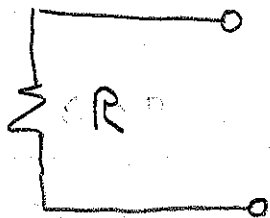

This resistor produces noise over a spectrum.

Place a filter next to the noise source

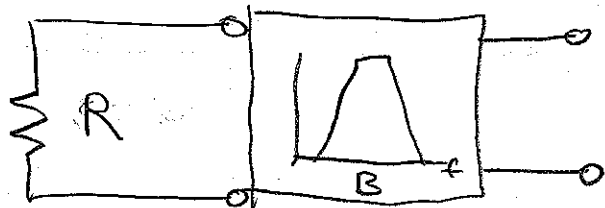

The filter has a bandwidth B .

To collect the maximum noise from the resistor, we must match the load impedance to the source impedance




SUBJECT

NAME

DATE

REVISION DATE

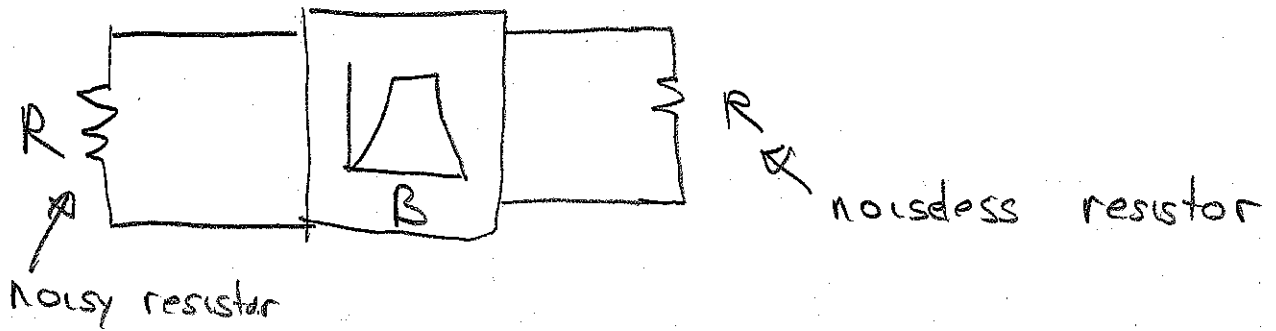


From Thermodynamics the average power available to the noiseless resistor

$$is \langle P_{av} \rangle = kTB$$

$$k = 13.6 \times 10^{-24} \text{ W/Kelvin/Hz}$$

$$or \quad k = -174 \text{ dBm/Hz at } T=293 \text{ K}$$

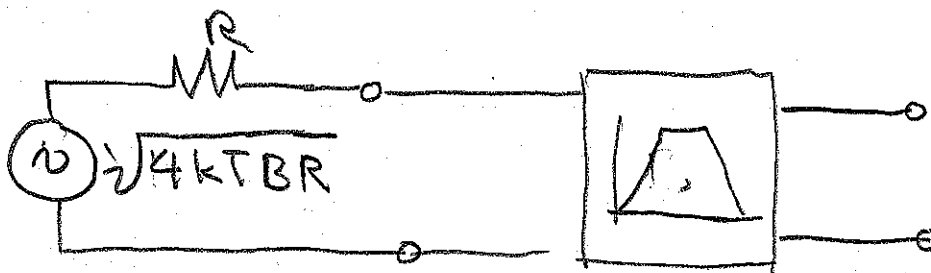An equivalent model for the noisy resistor is





SUBJECT

NAME

DATE

REVISION DATE

Why not just make R small and have no noise power?

Because to match the source to get the maximum power transfer, the load resistor would have to be made small so you can't win.

The available power density from a resistor is

$$S(f) = kT$$

No matter what the value of the resistance is!




SUBJECT

NAME

DATE

REVISION DATE

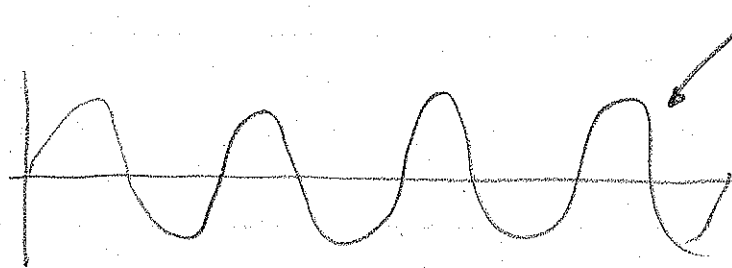
Consider a very small bandwidth ΔB a make a single measurement of the voltage deposited in the load resistor.



looks like a sine wave

because of the narrow filter.

Do another measurement

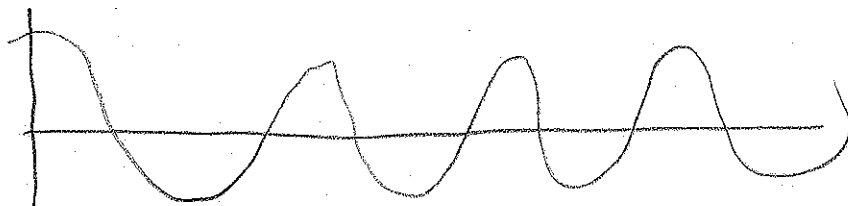

It has a different phase because its random.

The voltage on a given measurement is

$$V = \text{Re} \left\{ V_m e^{j\phi_m} e^{j\omega t} \right\}$$

$$V_m e^{j\phi_m} = V_{r_m} + j V_{i_m}$$



SUBJECT

NAME

DATE

REVISION DATE

The average value of the real or imaginary voltage is zero.

$$\langle V_r \rangle = \frac{1}{M} \sum V_{rm} = 0$$

$$\langle V_i \rangle = \frac{1}{M} \sum V_{im} = 0$$

The RMS is not zero

Since

$$\left\langle \frac{V^2}{R} \right\rangle = \left\langle \frac{V_r^2}{R} \right\rangle + \left\langle \frac{V_i^2}{R} \right\rangle = KTB$$

Then

$$\left\langle \frac{V_r^2}{R} \right\rangle = \frac{1}{R} \frac{1}{M} \sum V_r^2 = \frac{KTB}{2}$$

$$\left\langle \frac{V_i^2}{R} \right\rangle = \frac{1}{R} \frac{1}{M} \sum V_i^2 = \frac{KTB}{2}$$

Define $P_r^2 = \frac{V_r^2}{R}$ $\langle P_r^2 \rangle = \frac{KTB}{2}$

$P_i^2 = \frac{V_i^2}{R}$ $\langle P_i^2 \rangle = \frac{KTB}{2}$

$$\langle P_r^2 \rangle + \langle P_i^2 \rangle = \langle P \rangle = KTB$$



SUBJECT


NAME

DATE

REVISION DATE

Probability of a measurement
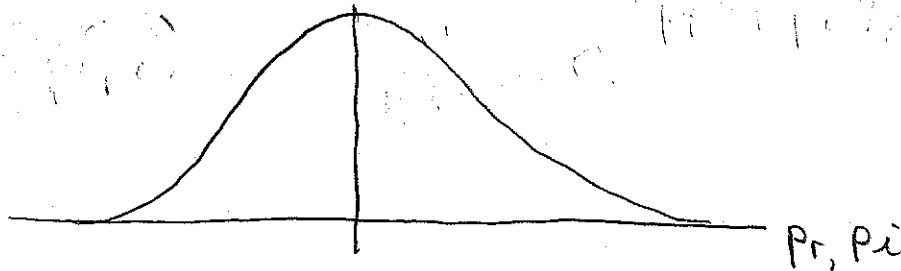
$$\psi(p) = \frac{1}{\sqrt{2\pi kTB}} e^{-\frac{1}{2} p^2 / kTB}$$




$$\psi(P) = \psi(p_r) \psi(p_i)$$

$$= \frac{1}{\pi kTB} e^{-\frac{(p_r^2 + p_i^2)}{kTB}} = \frac{1}{\pi kTB} e^{-\frac{P^2}{kTB}}$$

$$\langle \psi P \rangle = kTB$$

$$\langle \psi P^2 \rangle = (kTB)^2$$

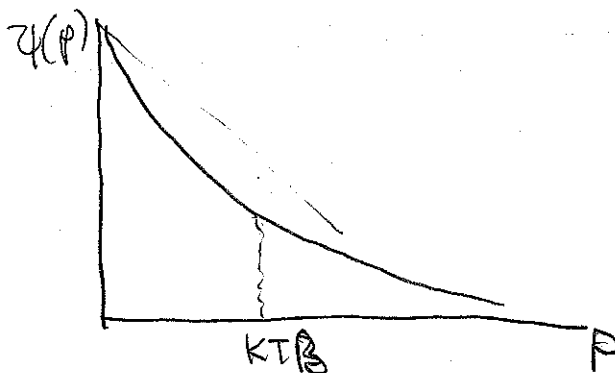

- 1) Most like value is 0
- 2) Average value is kTB
- 3) RMS value is kTB



SUBJECT


NAME

DATE

REVISION DATE

Noise in Amplifiers

Consider

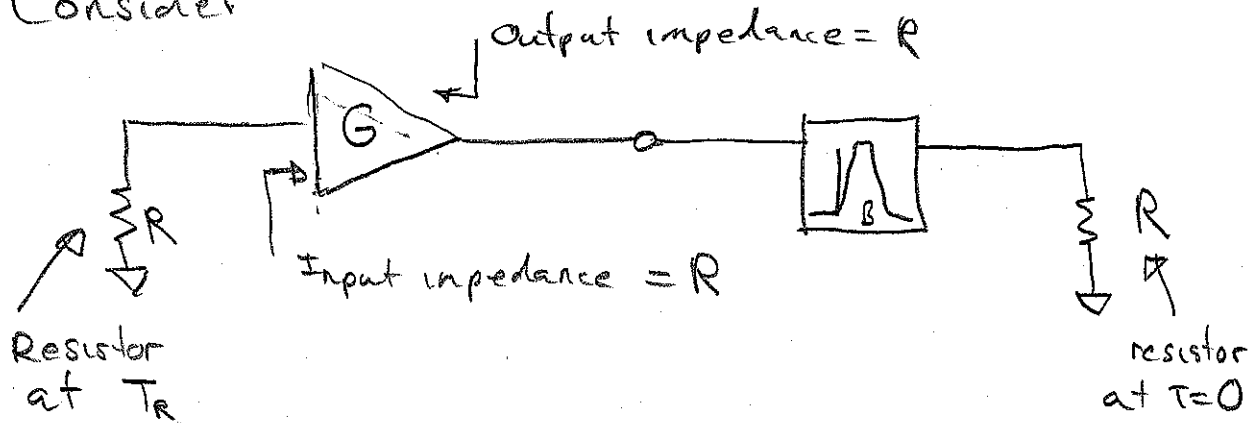

$G =$ power Gain

What is the power received into the noiseless resistor?

If the amplifier is noiseless then:

$$P_r = G k T_R B$$

If the amplifier has noise, we always, always, define the noise measured on the output; referred to the input

$$P_A = G k T_A B$$

measured on output referred to input



SUBJECT

NAME

DATE

REVISION DATE

T_A is not an actual temperature, but an effective temperature.

The noise figure is defined as.

$$N_f = \frac{P_A + P_R|_{293K}}{P_R|_{293K}}$$

The noise figure is typically referred to in dB (because it is a power ratio)

The noise figure can never be lower than 0 dB.

$$P_A = P_R|_{293K} (N_f - 1)$$

$$T_A = 293K (N_f - 1)$$

IF $N_f = 2$ (3 dB)

$$T_A = 293K$$

$$N_F = N_A = 0.7 \text{ dB}$$

$$N_F = 1.175$$

$$T_A = 51 \text{ K}$$

Example

The noise floor of a spectrum analyzer measured with its input terminated in 50Ω is -90 dBm . The resolution bandwidth is 1 MHz .

a) What is the noise figure of the SA

b) What is the noise Temp of the SA

$$P_m = -90 \text{ dBm into } 1 \text{ MHz}$$

$$\therefore P_m = (-90 - 60) \text{ dBm} = -150 \text{ dBm into } 1 \text{ Hz}$$

$$-60 = 10 \log_{10} \left(\frac{1 \text{ Hz}}{1 \text{ MHz}} \right)$$

$$P_{R|_{293}} = -174 \text{ dBm into } 1 \text{ Hz}$$

$$P_m = P_{SA} + P_{R|_{293K}}$$

$$N_F = P_m / P_{R|_{293K}}$$

$$N_{F_{dB}} = -150 \text{ dBm} - (-174 \text{ dBm}) = 24 \text{ dBm}$$

$$T_{SA} = 73,300 \text{ K} !!$$



SUBJECT


NAME

DATE

REVISION DATE

Measuring Noise Figure

Simple (Error prone way)

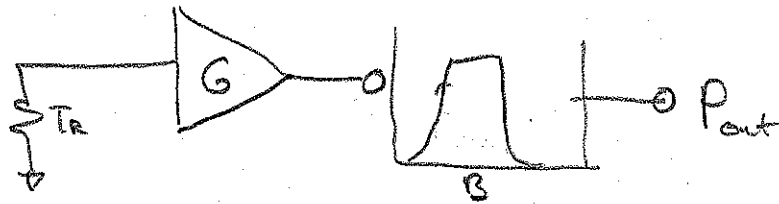

Measure G with a network analyzer

Measure P_{out} with a spectrum analyzer

$$P_o = G k T_R B + G k T_A B$$

$$\frac{P_o}{G} = k T_R B + k T_A B$$

$$\frac{P_{out}}{G k T_R B} = \frac{k T_R B + k T_A B}{k T_R B} = N_f$$

Need to know G precisely

Need to know B precisely.




SUBJECT

NAME


DATE

REVISION DATE

2nd Technique (Y factor)

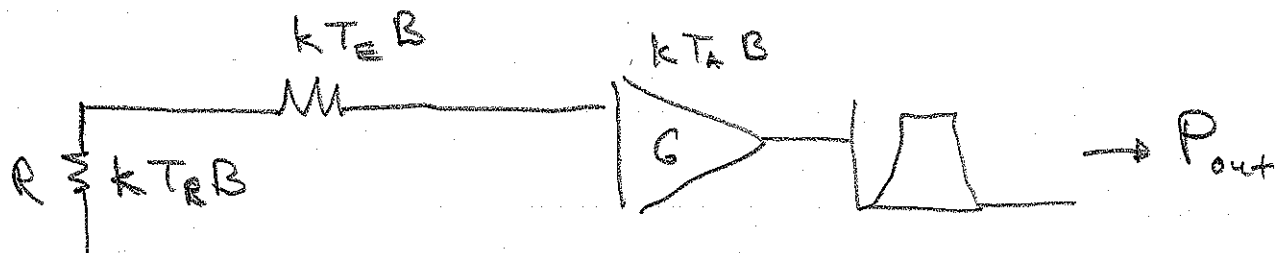

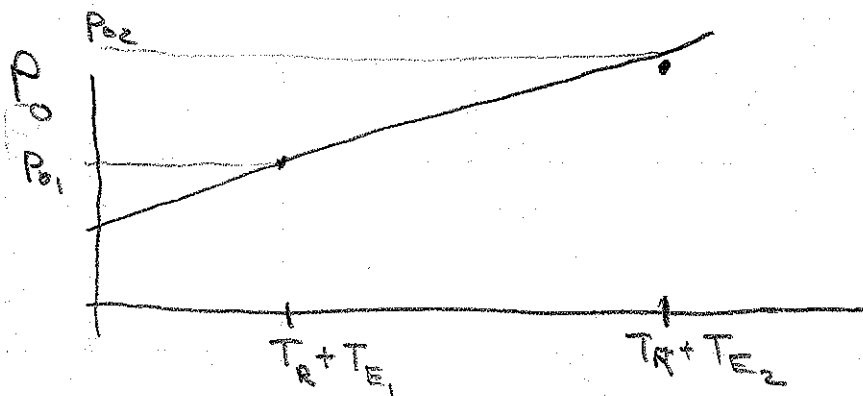Assume I can change T_E
Make two measurements T_{E1} & T_{E2}



Find the intercept = Power added by Amp

$$P_o = \frac{P_{o2} - P_{o1} (T - T_R - T_{E1})}{T_{E2} - T_{E1}} + P_{o1}$$

$$P_{int} = P_{o1} - \frac{(T_R + T_{E1}) (P_{o2} - P_{o1})}{(T_{E2} - T_{E1})}$$

$$T_1 = T_r + T_{E1}$$

$$T_2 = T_r + T_{E2}$$

$$T_r = T_1 - T_{E1}$$

$$P_o = \frac{\Delta P}{\Delta T} (T - T_1) + P_{o1}$$

$$N_f = \frac{P_o|_{T=T_r}}{P_o|_{T=T_r} - P_o|_{T=0}}$$

$$P_o|_{T=T_r} = P_{o1} - \frac{\Delta P T_{E1}}{\Delta T}$$

$$P_o|_{T=0} = P_{o1} - \Delta P \frac{T}{\Delta T}$$

$$P_o|_{T=T_r} - P_o|_{T=0} = \frac{\Delta P}{\Delta T} (T_1 - T_{E1})$$

$$N_f = \frac{P_{o1} - \frac{\Delta P}{\Delta T} T_{E1}}{\frac{\Delta P}{\Delta T} (T_1 - T_{E1})}$$

$$N_f = \frac{P_{o1}}{\Delta P} \frac{\Delta T}{(T_1 - T_{E1})} - \frac{T_{E1}}{(T_1 - T_{E1})}$$


For T_{E1} small

$$N_f = \frac{P_{o1}}{\Delta P} \frac{\Delta T}{T_r}$$

Noise figure of Systems

$$N_f = \frac{P_R + P_A}{P_R}$$

$$(N_f - 1)P_R = P_A$$

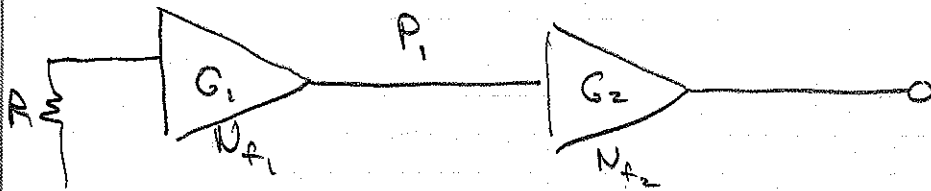

$$P_1 = G_1(P_R + P_{A1})$$

$$P_2 = G_1 G_2 (P_R + P_{A1}) + G_2 P_{A2}$$

$$P_2 = G_1 G_2 P_R + G_1 G_2 (N_{f1} - 1)P_R + G_2 (N_{f2} - 1)P_R$$

$$N_{f_{total}} = \frac{P_2 / G_1 G_2}{P_R}$$

$$N_{f_{total}} = N_{f1} + \frac{N_{f2} - 1}{G_1}$$

$$N_{f_{total}} = N_{f1} + \frac{N_{f2} - 1}{G_1} + \frac{N_{f3} - 1}{G_1 G_2}$$

Example

$$G_1 = 20 \text{ dB}$$

$$N_{f1} = 0.7 \text{ dB}$$

$$G_2 = 20 \text{ dB}$$


$$N_{f2} = 3 \text{ dB}$$

$$N_{f2} = 2$$

$$G_1 = 10$$

$$N_{f \text{ total}} = 0.7 + \frac{2-1}{10} = 0.8 !$$

Noise Figure of an Attenuator

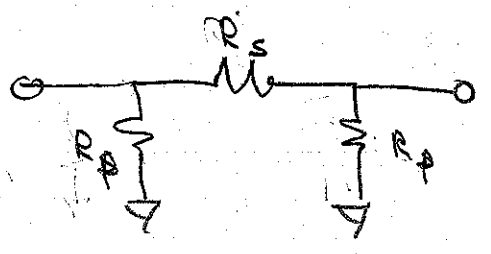

for 6 dB

$$R_s = 37 \Omega$$


$$R_p = 150 \Omega$$

for 20 dB

$$R_s = 247 \Omega$$

$$R_p = 61 \Omega$$

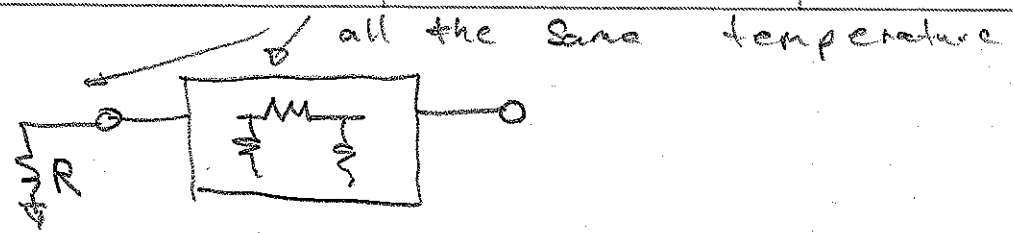So an attenuator is just a resistor network



Attenuation = A

What is the power on the output

$$P_o = k T_r B$$

Refer to this to the input

$$G = \frac{1}{A}$$

$$P_o \Big|_{\text{input}} = A k T_r B$$

$$N_f = \frac{A k T_r B}{k T_r B} = A$$

A 3dB attenuator has a noise figure of 3dB

Example



$$G_1 = 20 \text{ dB}$$

$$N_1 = .7 \text{ dB} \Rightarrow 1.175$$

$$N_{\text{Att}} = 3 \text{ dB} \Rightarrow 2$$

$$G_{\text{Att}} = 1/2$$

$$N_{\text{Total}} = 2 + \frac{1.175 - 1}{1/2}$$

$$= 2 + .35$$

$$= 2.35$$

$$= 3.711 \text{ dB}$$

$$T_{\text{eff}} = 395 \text{ K}$$